

HB 219 Worked Example 3.4.1 Fault at 33 kV Concrete or Steel Pole

5 km aerial HV feed, no OHEW.

33 kV source, no NER.

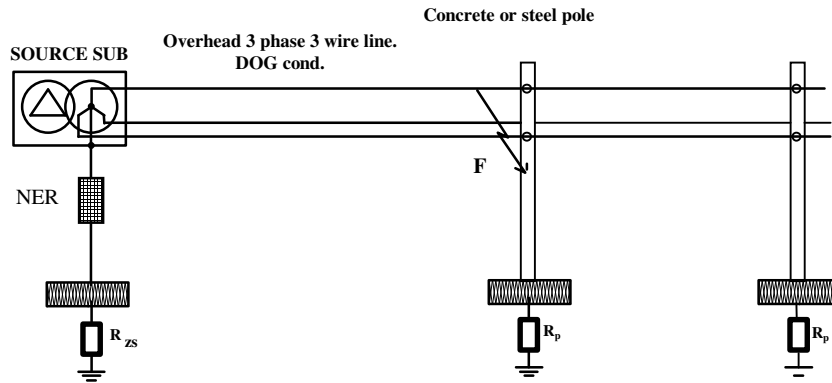


Fig. 3.4.1.1 Fault at 33kV concrete or steel pole

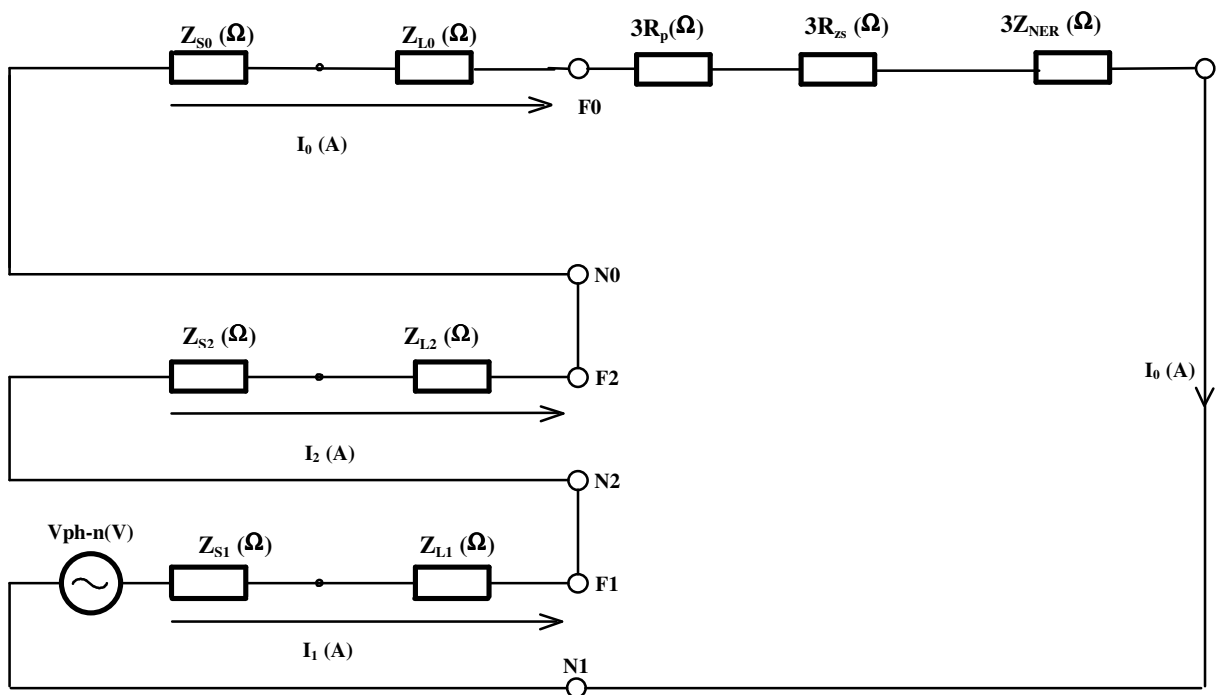


Fig. 3.4.1.2 Symmetrical components network for a HV single phase to earth fault at the pole.

33kV SYSTEM DATA

SOURCE VOLTAGE (volts) & IMPEDANCE (Ohms)

Single phase source voltage V_{ph-n} (Volts) $V_{S1} := 19053$

Single Phase Fault Level S (MVA) $S := 500$

Source impedance calculated from the fault level. Assume source impedance is purely reactive and positive sequence = negative sequence = zero sequence impedance.

Positive sequence source impedance (Ohms) $Z_{S1} := \frac{33^2}{S} \cdot j$ $Z_{S1} = 2.178j$

Negative sequence source impedance (Ohms) $Z_{S2} := Z_{S1}$

Zero sequence source impedance (Ohms) $Z_{S0} := Z_{S1}$

33kV Overhead line impedance

Conductor size: DOG (6/4.72mm aluminium with 7/1.57mm steel)

Length (km) $L := 5.0$

Line sequence impedance (Ohms/km)

Positive sequence line impedance (Ohms/km) $Z_{L1} := 0.2722 + 0.3479j$

Negative sequence line impedance (Ohms/km) $Z_{L2} := Z_{L1}$


Zero sequence line impedance (Ohms/km) $Z_{L0} := 0.4204 + 1.5748j$

33kV NER AND EARTHING IMPEDANCE (Ohms).

Neutral Earthing Resistor (Ohms) $Z_{NER} := 0$

Zone substation earthing system resistance (Ohms) $R_{zs} := 0.01$

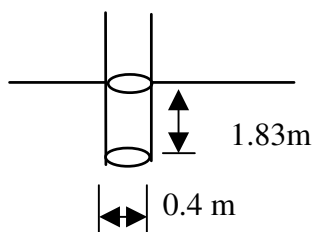Surface soil resistivity (Ohm-m) $\rho := 10$



Each pole 1.83 m deep in soil and 0.4 m dia.

Pole earth resistance (Ohms) $R_p := 0.248 \cdot \rho$ $R_p = 2.480$

The equivalent hemispherical radius (m) $r_E := \frac{\rho}{2 \cdot \pi \cdot R_p}$ $r_E = 0.642$

CALCULATIONS

One Phase to Earth fault on the 33kV feeder at a conductive pole

Sequence network impedance (Ohms)

$$\begin{aligned} Z_{\text{pos}} &:= Z_{S1} + Z_{L1} \cdot L & Z_{\text{neg}} &:= Z_{S2} + Z_{L2} \cdot L & Z_{\text{zero}} &:= Z_{S0} + Z_{L0} \cdot L + 3 \cdot R_p + 3 \cdot R_{zs} \\ Z_{\text{pos}} &= 1.361 + 3.918j & Z_{\text{neg}} &= 1.361 + 3.918j & Z_{\text{zero}} &= 9.572 + 10.052j \end{aligned}$$

Zero sequence fault current (Amps)

$$I_0 := \frac{V_{s1}}{Z_{\text{pos}} + Z_{\text{neg}} + Z_{\text{zero}} + 3 \cdot Z_{\text{NER}}}$$

Fault current (Amps)

$$I_f := 3 \cdot I_0 \quad I_f = 1491.7 - 2170.3j \quad |I_f| = 2633.5$$

The EPR at the conductive pole (Volts)

$$EPR_{\text{pole}} := I_f \cdot R_p \quad |EPR_{\text{pole}}| = 6531$$

